


As-of May 2015


C.Ott

## Full Spectrum Cutter

Logic Levels

(during a  
raster cut)

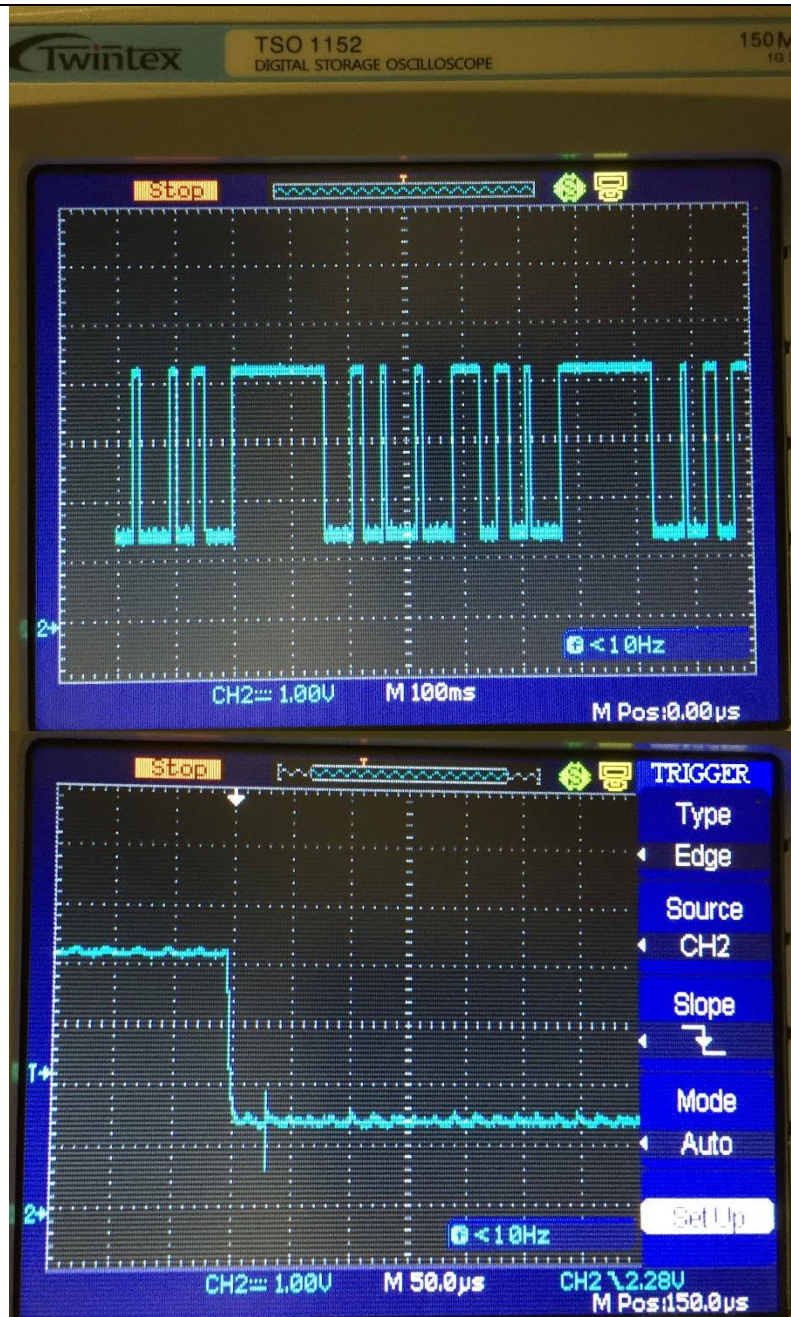


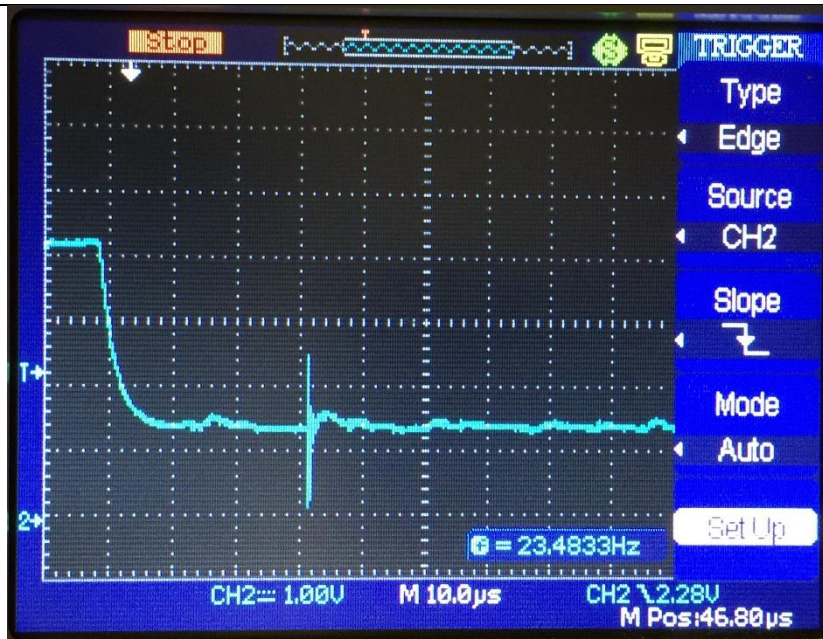

Twisted triple pig-tail


With a keyed connector

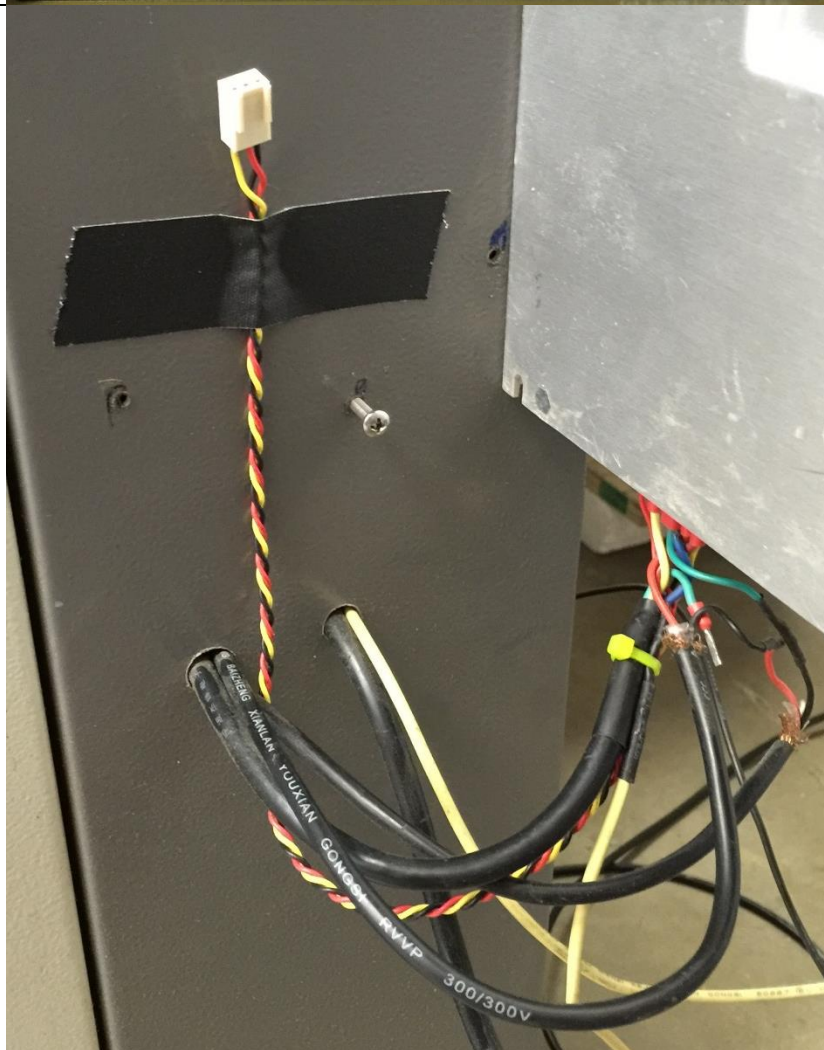
Note:  
Interface card  
located  
physically  
close to the  
power supply





Kludgy  
Construction

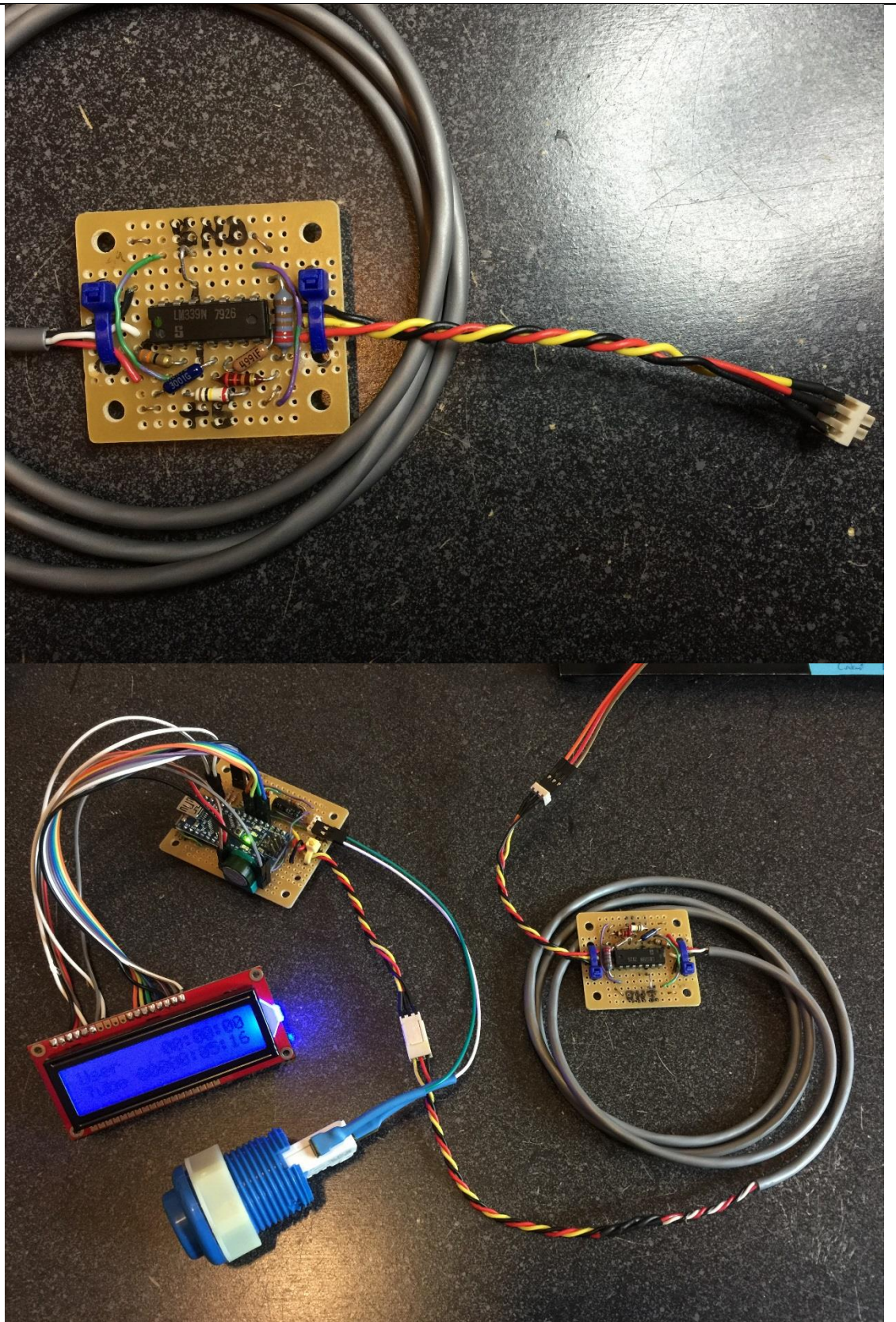

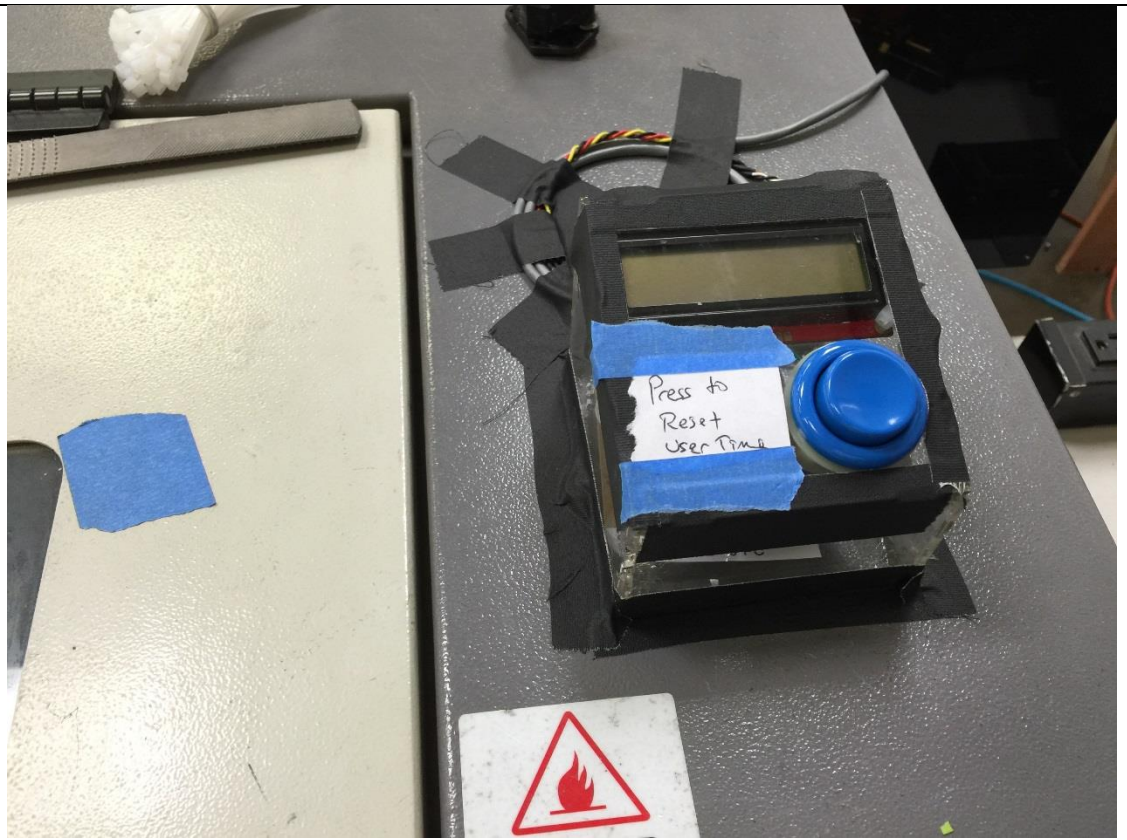



# LaserSaur

Logic Levels

